
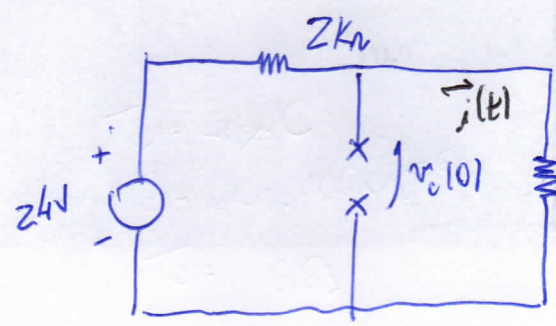


3

1º Passo $i(t) = K_1 + K_2 \cdot e^{-\frac{t}{\tau_0}}$

2º Passo

$p/t < 0$

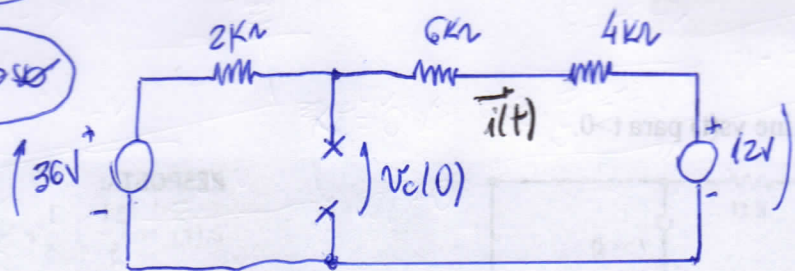


$$V_R(0) = \frac{10k}{10k + 2k} \cdot 24$$

$$V_R(0) = \frac{10k}{12k} \cdot 24^2$$

$$V_R(0) = 20V$$


Voltagem:

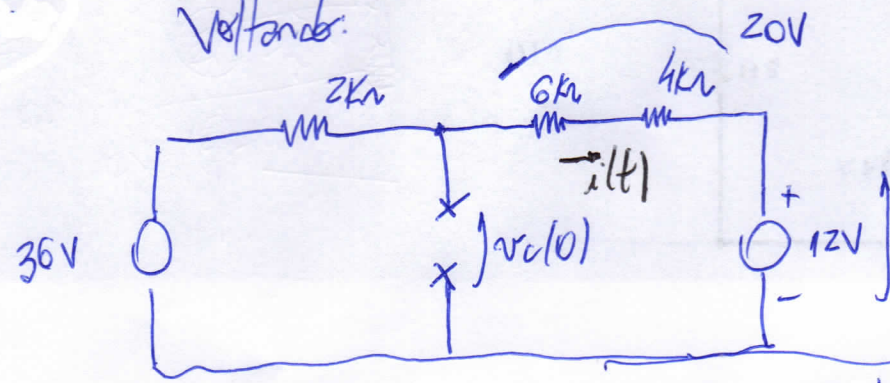

$$v_C(0) = 20 + 12 = 32V$$

3º Passo

$p/t \rightarrow 0$

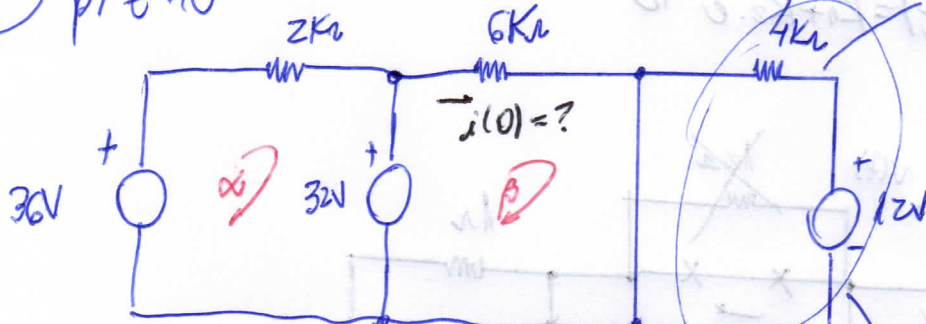

Corrente existe mas não interessa

na carga pois tem fonte (desprezar)

$$6k\beta = 32$$


$$\beta = \frac{32}{8 \times 10^3} = \frac{16}{3} \text{ mA}$$

$$i(0) = \frac{16}{3} \text{ mA}$$

$$i(0) = 5,33 \text{ mA}$$

4º Passo

$p/t \rightarrow \infty$

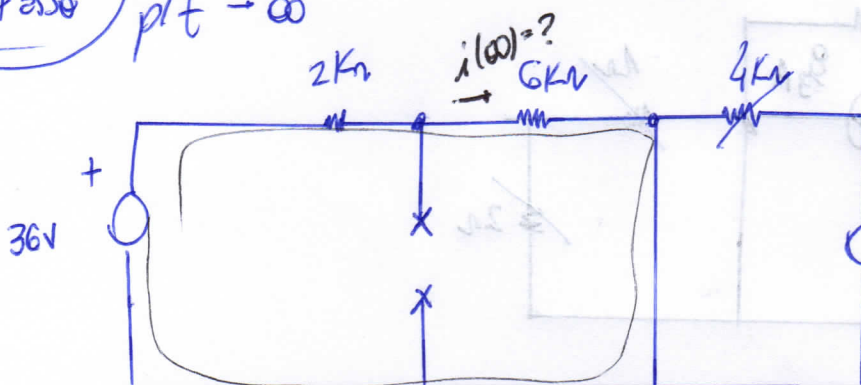

$$i(\infty) = \frac{36}{8 \times 10^3} \rightarrow \boxed{i(\infty) = \frac{9}{2}} \quad \boxed{i(\infty) = 4,5 \text{ mA}}$$

5º Passo

$T_c = ?$

$$T_c = R_{th} \cdot C$$

$$R_{th} = 2k \parallel 6k = \frac{2 \times 6}{2 + 6} = \frac{12}{8} = \frac{3}{2} k\Omega$$

$$T_c = \frac{3 \cdot 10^3 \cdot 100 \times 10^{-6}}{2}$$

$$\boxed{T_c = 0,15 \text{ s}}$$

6º Passo

$$i(0) = K_1 + K_2 = \frac{16}{3} \text{ mA}$$

$$i(\infty) = K_1 = \frac{9}{2} \text{ mA}$$

$$\therefore K_1 = \frac{9}{2} \text{ mA}$$


$$K_2 = \frac{16}{3} - \frac{9}{2}$$

$$K_2 = \frac{32 - 27}{6} = \frac{5}{6} \text{ mA}$$

$$\boxed{i(t) = \frac{9}{2} + \frac{5}{6} \cdot e^{-\frac{t}{0,15}} \text{ [mA]}}$$

④ 1ª Passo $v(t) = K_1 + K_2 \cdot e^{-\frac{t}{\tau_0}}$

2ª Passo $p/t < 0$

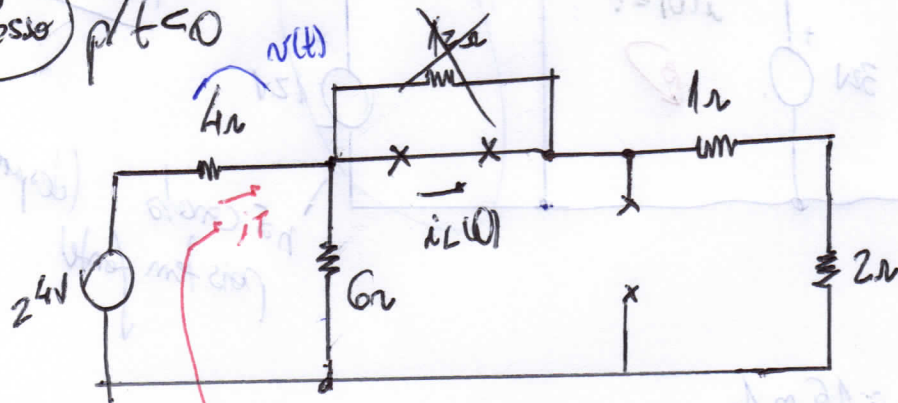

$$i_T = \frac{24}{6} = 4A$$



$$i_L(0) = \frac{6}{6+3} \cdot 4$$

$$i_L(0) = \frac{2}{3} \cdot 4$$

$$i_L(0) = \frac{8}{3}A$$

3ª Passo

$p/t > 0$

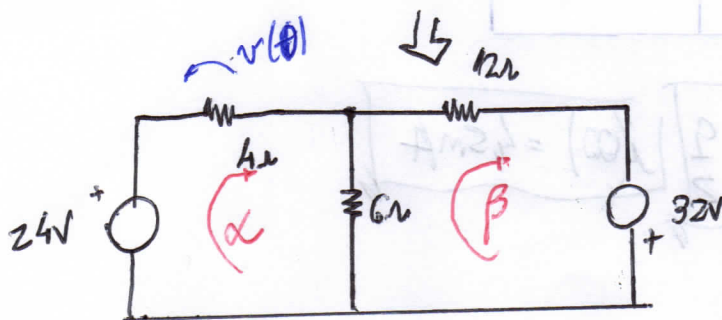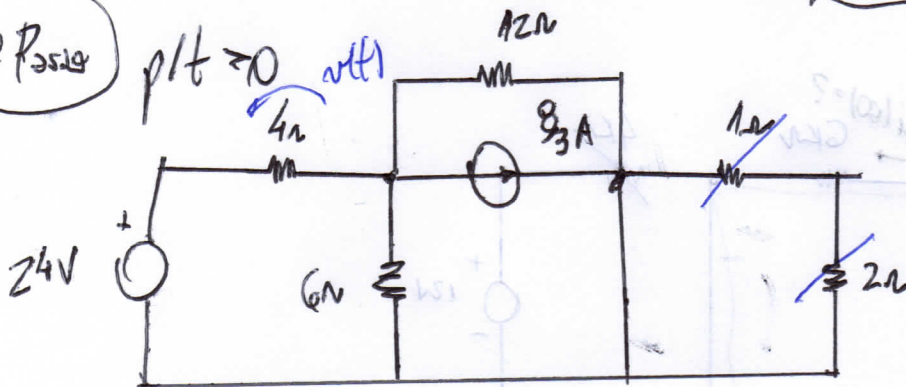


$$\begin{aligned} 10\alpha - 6\beta &= 24 \quad \times 3 \\ -6\alpha + 18\beta &= 32 \\ \hline 24\alpha &= 104 \end{aligned}$$

$$\alpha = \frac{104}{24} = \frac{13}{3} = 4,33A$$

$$v(t) = 4 \cdot \frac{13}{3} = \frac{52}{3}V$$


$$v(0) = \frac{52}{3}V$$

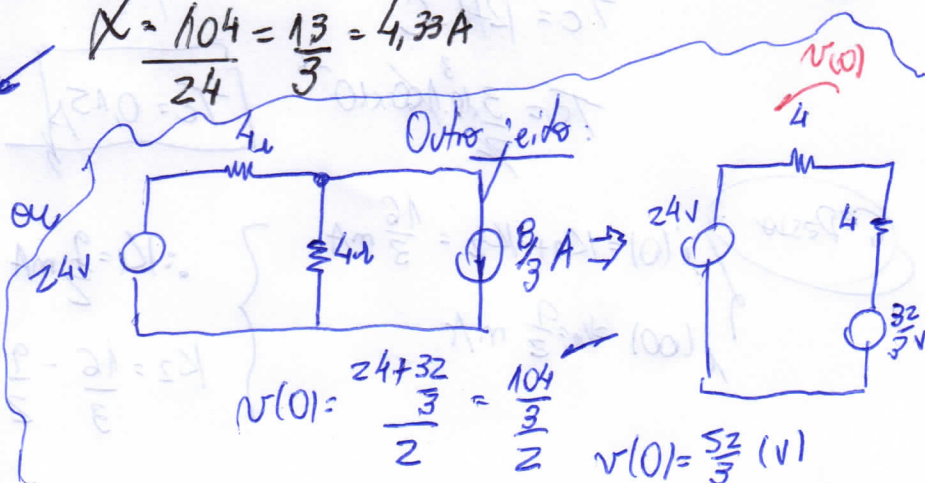

$$v(0) = \frac{24+32}{2} = \frac{104}{2} = \frac{52}{3}V$$


$$v(0) = \frac{52}{3}(V)$$

4^o Passo

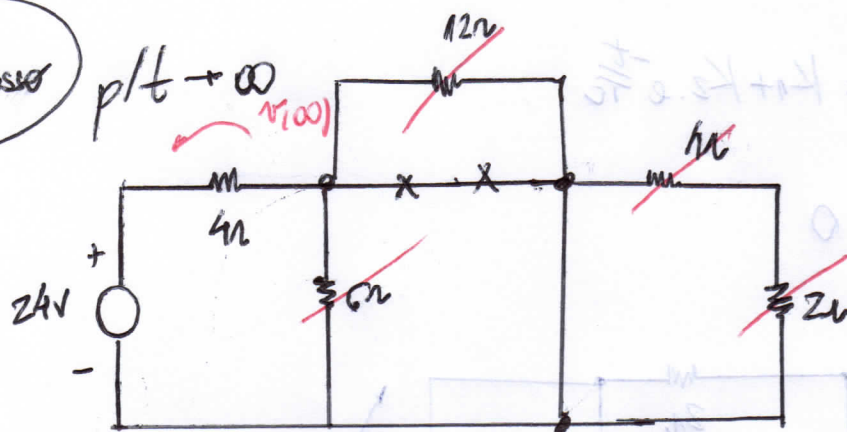

$$v(\infty) = 24V$$

5^o Passo

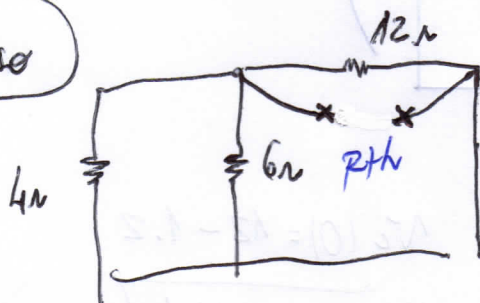

$$R_{th} = 12 \parallel 6 \parallel 4$$

$$R_{th} = \left(\frac{12 \cdot 6}{12 + 6} \right) \parallel 4$$

$$R_{th} = 4 \parallel 4 \quad \boxed{R_{th} = 2\Omega}$$

$$T_c = \frac{L}{R_{th}} = \frac{4}{2} \quad T_c = 2s$$

6^o Passo

$$v(0) = K_1 + K_2 = \frac{52}{3}$$

$$v(\infty) = 24 = K_1$$

$$\therefore K_1 = 24$$

$$K_2 = \frac{52}{3} - 24$$

$$K_2 = \frac{52 - 72}{3} = -\frac{20}{3}$$


$$\therefore v(t) = 24 - \frac{20}{3} e^{-\frac{t}{2}} [V]$$

5 1° Passo

$$v_s(t) = K_1 + K_2 \cdot e^{-\frac{t}{\tau_c}}$$

2° Passo

$p/t < 0$

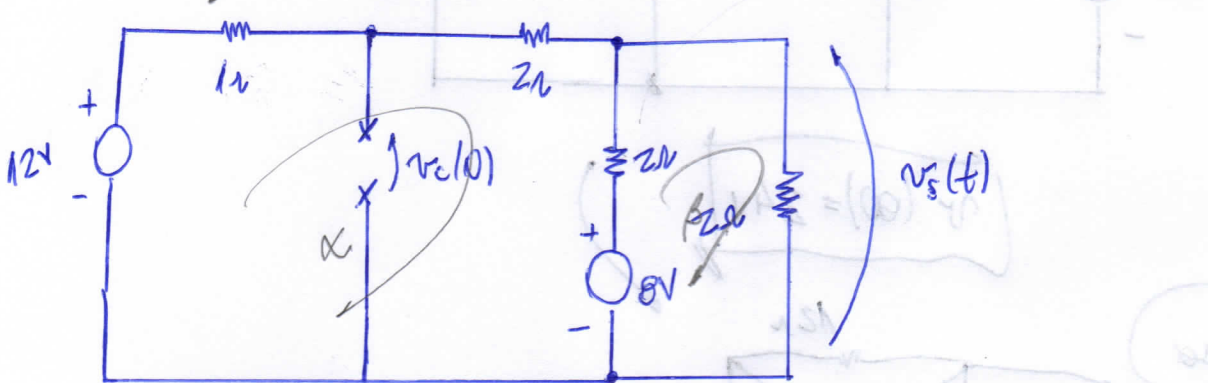

$$\begin{cases} 5\alpha - 2\beta = 12 - 8 \quad (2) \\ -2\alpha + 4\beta = 8 \end{cases}$$


$$8\alpha = 16 \quad \alpha = \frac{16}{8} \quad \boxed{\alpha = 2A}$$

$$v_c(0) = 12 - 1 \cdot 2$$

$$\boxed{v_c(0) = 10V}$$

3° Passo

$p/t \geq 0$

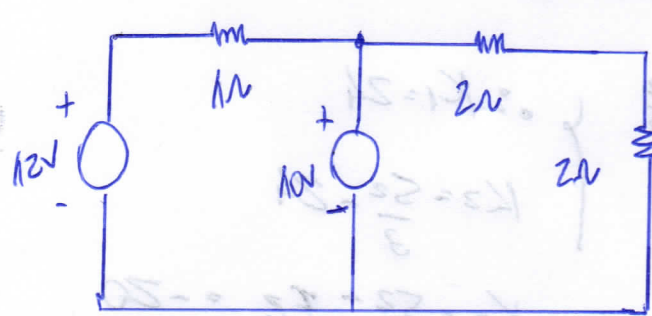


$$v_s(0) = ?$$

$$v_s(0) = \frac{2}{2+2} \cdot 10$$

$$\boxed{v_s(0) = 5V}$$

4° Passo

$p/t \rightarrow \infty$

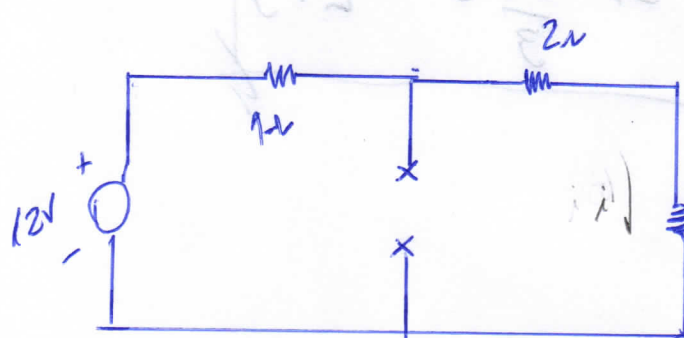

$$v_s(\infty) = ?$$

$$i = \frac{12}{5} A$$

Logo: $v_s(\infty) = 2 \cdot \frac{12}{5}$

$$\boxed{v_s(\infty) = \frac{24}{5} [V]}$$

5^o passo $T_c = ?$


$$T_c = R_{eq} \cdot C$$

$$R_{eq} = 4 \Omega // 1 \Omega$$

$$T_c = \frac{4}{5} \cdot 2$$

$$T_c = \frac{8}{5} \text{ s}$$
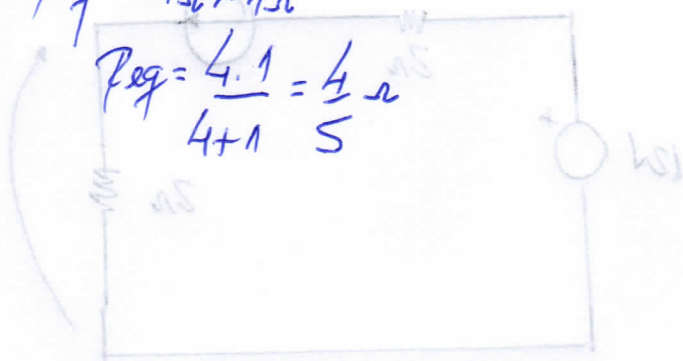
$$R_{eq} = \frac{4 \cdot 1}{4+1} = \frac{4}{5} \Omega$$



6^o passo $\left\{ \begin{array}{l} v_s(0) = K_1 + K_2 = 5 \\ v_s(\infty) = K_1 = \frac{24}{5} \end{array} \right.$

$$\therefore K_1 = \frac{24}{5}$$


$$K_2 = 5 - \frac{24}{5}$$

$$K_2 = \frac{25-24}{5} \quad \left| K_2 = \frac{1}{5} \right|$$

$$\text{Logo: } v_s(t) = \frac{24}{5} + \frac{1}{5} \cdot e^{-\frac{t}{8}} \text{ [V]}$$

6 1^o passo $v_s(t) = K_1 + K_2 \cdot e^{-\frac{t}{T_c}}$

2^o passo p/t qd

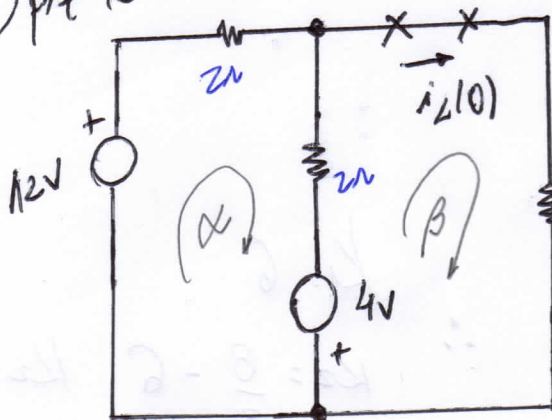


$$v_x(t) = ?$$

$$\begin{cases} 4\alpha - 2\beta = 12 + 4 \\ -2\alpha + 4\beta = -4 \end{cases} \quad (2)$$

$$\beta = \frac{8}{6}$$

$$i_L(0) = \frac{8}{6} \text{ A}$$


3º passo $p/t > 0$

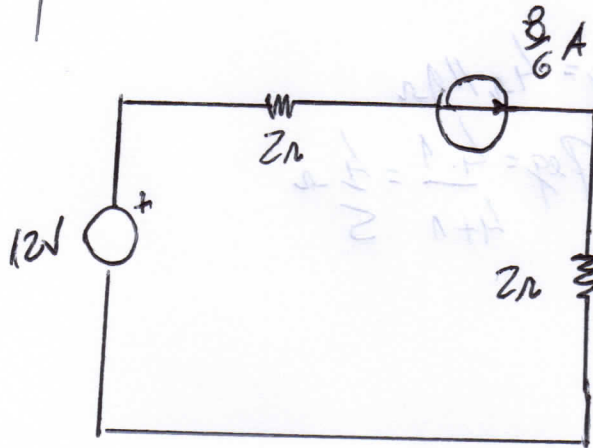

$v_s(t)$

$$v_s(0) = \frac{8}{6} \cdot 2 = \frac{16}{6} = \frac{8}{3} \text{ [V]}$$

4º passo $p/t \rightarrow \infty$

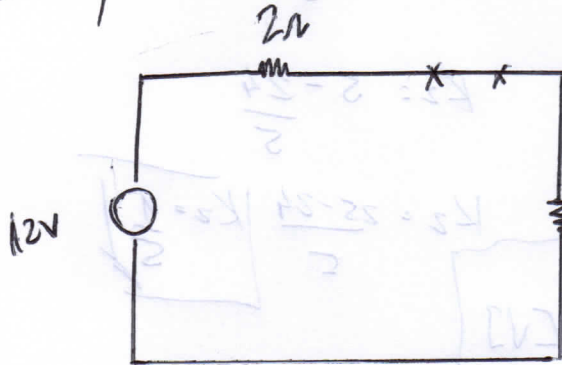

$v_s(\infty)$

$$v_s(\infty) = 6 \text{ V}$$

$$v_s(\infty) = \frac{2}{2+2} \cdot 12$$

5º passo $T_c = \frac{L}{R_{eq}}$

$$R_{eq} = R_{th} = 4\Omega \quad (2+2)$$

$$T_c = \frac{L}{R} = \frac{1}{2} \text{ s}$$

6º passo

$$\begin{cases} v(0) = K_1 + K_2 = \frac{8}{3} \\ v(\infty) = K_1 = 6 \end{cases}$$

$$K_1 = 6$$

$$K_2 = \frac{8}{3} - 6$$

$$K_2 = \frac{8-18}{3}$$

$$K_2 = -\frac{10}{3}$$

$$v_s(t) = 6 - \frac{10}{3} e^{-2t} \text{ [V]}$$