

① fugir das fontes de corrente (dependentes e independentes) ①

$$\begin{cases} 2\alpha + 3\beta - 3\gamma = 12 \text{ (I)} \end{cases}$$

$$\text{Sabe-se que: } \begin{cases} \alpha - \beta = 2 \text{ (II)} \\ \gamma = -4 \text{ A (III)} \end{cases} \rightarrow \alpha = 2 + \beta$$

$$I_0 = \alpha - \gamma \text{ (IV)}$$

II em I e IV em I

$$2 \cdot (2 + \beta) + 3\beta - 3 \cdot (-4) = 12$$

$$4 + 2\beta + 3\beta + 12 = 12$$

$$5\beta = -4$$

$$\boxed{\beta = -\frac{4}{5} \text{ A}}$$

Logo: $\alpha = 2 + \beta$

$$\alpha = 2 - \frac{4}{5}$$

$$\alpha = \frac{10 - 4}{5}$$

$$\boxed{\alpha = \frac{6}{5} \text{ A}}$$

Deito forma:

$$I_0 = \alpha - \gamma$$

$$I_0 = \frac{6}{5} - (-4)$$



$$I_0 = \frac{6 + 20}{5} = \frac{26}{5} = 5,2 \text{ A}$$

$$\therefore \boxed{I_0 = 5,2 \text{ A}}$$

② * Transformação de Fonte
para achar E_{th}

Determinação de R_{th}







Retorno

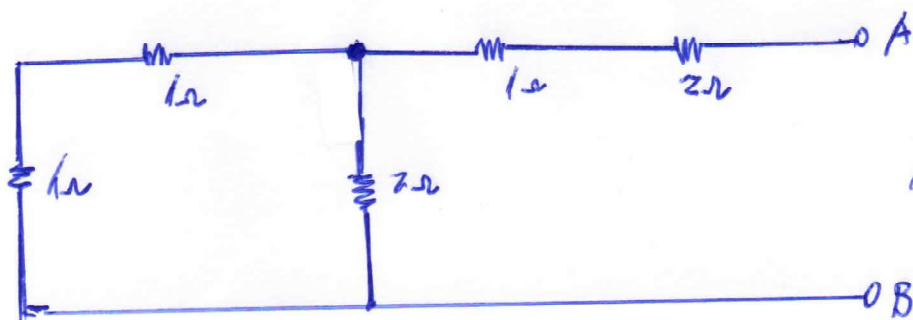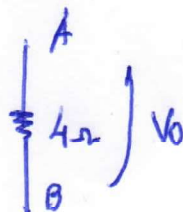

$$R_{th} = 4 \Omega$$


Determinar E_{th} :

(2)

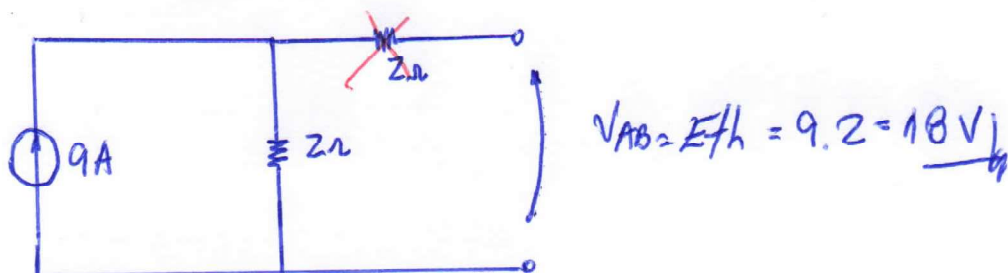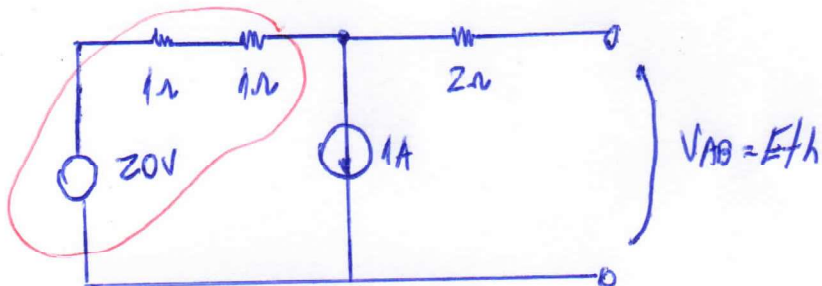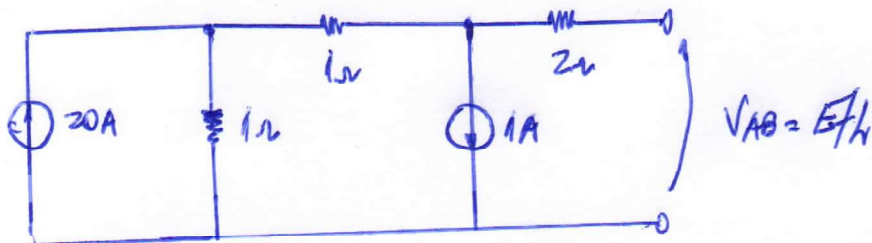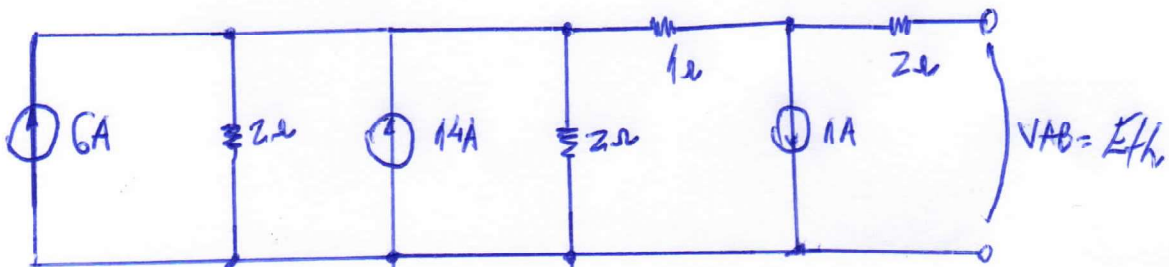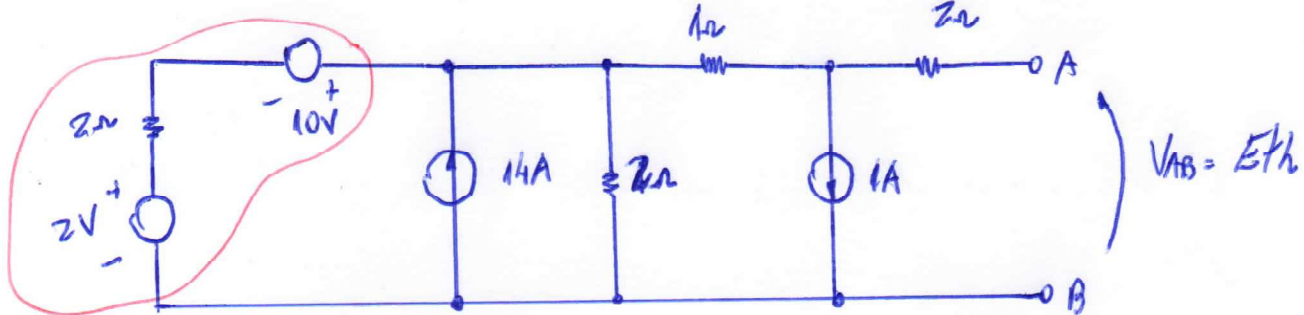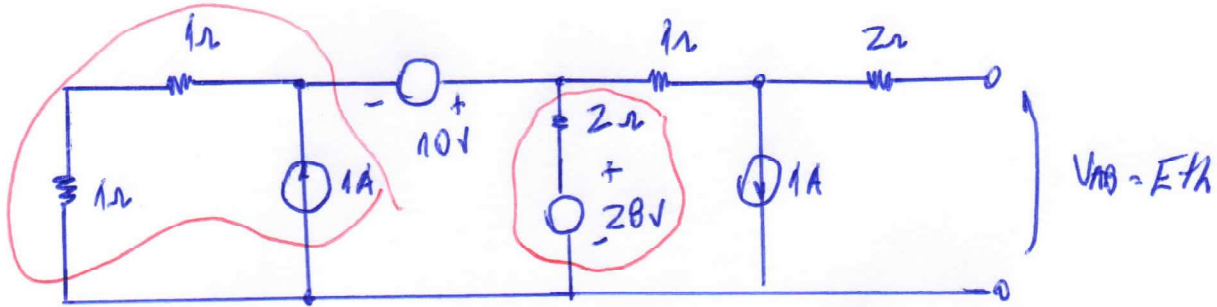

Desenhar o Circuito Equivalente

3

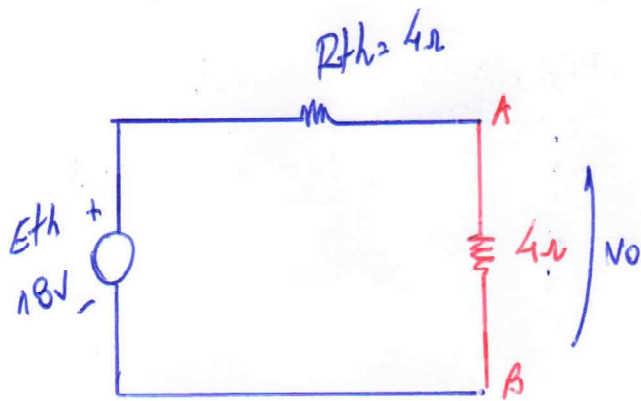


Divisor de Tensão

$$V_{AB} = V_0 = \frac{4}{4+4} \cdot 18 = 9V$$

$$\boxed{V_0 = 9V}$$

3 Influência de 36 V - V_{01} :

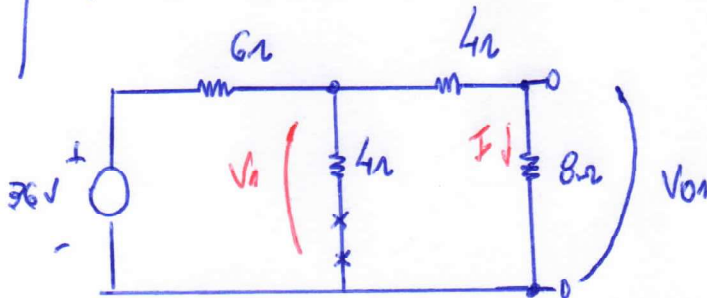

$$R_{eq I} = (8+4) \parallel 4$$

$$R_{eq I} = \frac{12 \cdot 4}{12+4} = \frac{48}{16} = 3\Omega$$

Divisor de Tensão

$$V_{01} = \frac{3}{3+6} \cdot 36$$


$$\boxed{V_{01} = 3 \cdot 4 = 12V}$$

Logo $V_{01} = ?$

$$V_{01} = \frac{8}{8+4} \cdot 12$$

$$\boxed{V_{01} = 8V}$$

Influência de 48V - V_{02} :

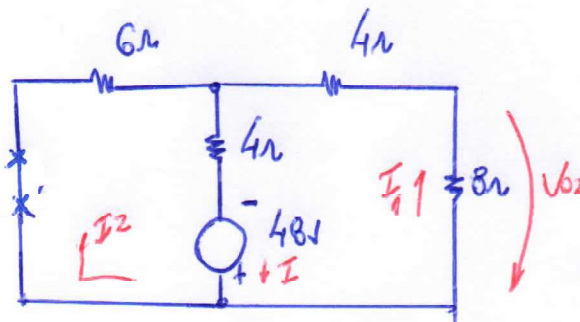

$$R_{eq I} = 12 \parallel 6 + 4$$

$$R_{eq I} = 8\Omega$$

$I_{total} = ?$

$$I = \frac{48}{8} = 6A$$

$R_{eq I}$

Divisor de Corrente

$$I_1 = \frac{6}{12+6} \cdot I$$

$$I_1 = \frac{6}{18} \cdot 6 \quad I_1 = 2A$$

Logo: $V_{02} = 8 \cdot I_1$

$$V_{02} = 8 \cdot 2$$

$$V_{02} = 16V$$

Finalmente:


$$V_0 = V_{01} + V_{02}$$

$$V_0 = 8 - 16$$

$$\boxed{V_0 = -8V}$$

©

(4)

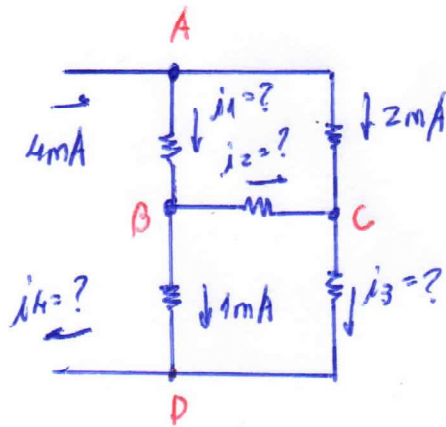

no A: $-4 + i_1 + 2 = 0$

$i_1 = 4 - 2 \quad \boxed{i_1 = 2 \text{ mA}}$

no B: $-i_1 + i_2 + 1 = 0$

$-2 + i_2 + 1 = 0$

$i_2 = 2 - 1$

$\boxed{i_2 = 1 \text{ mA}}$

no C:

$-2 - i_2 + i_3 = 0$

$-2 - 1 + i_3 = 0$


$\boxed{i_3 = 3 \text{ mA}}$

no D:

$i_4 - 1 - 3 = 0$

$\boxed{i_4 = 4 \text{ mA}}$

(5)

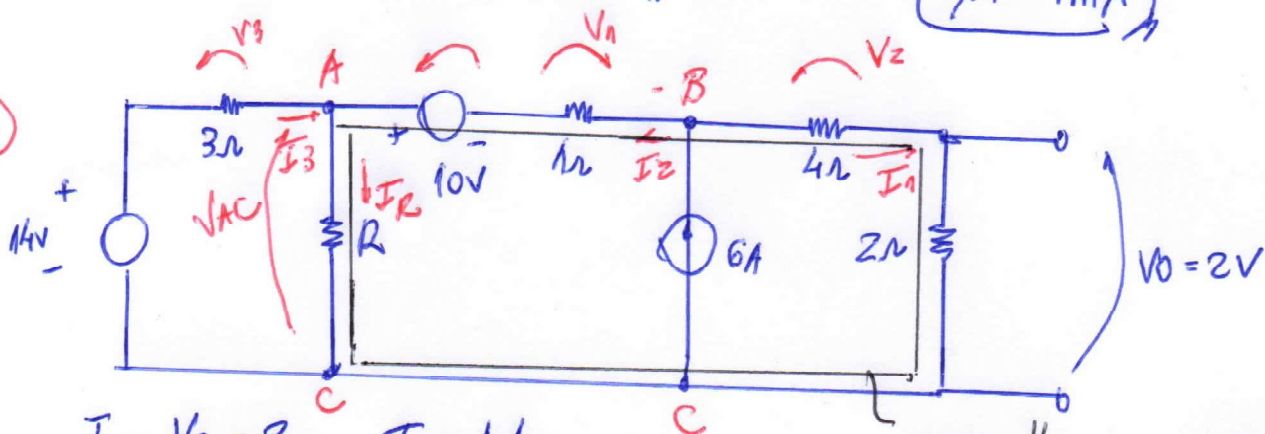

$I_1 = \frac{V_0}{2} = \frac{2}{2} \quad I_1 = 1 \text{ A}$

no B: $I_2 + I_1 - 6 = 0$

$I_2 = 6 - 1$

$\boxed{I_2 = 5 \text{ A}}$

Supermalha: LKT

$V_{AC} - 10 + V_1 - V_2 - V_0 = 0$

$V_{AC} = 10 - V_1 + V_2 + V_0$

$V_{AC} = 10 - 5 \cdot 1 + 4 \cdot 1 + 2$

$V_{AC} = 10 - 5 + 6$

$\boxed{V_{AC} = 11 \text{ V}}$

Supermalha

$14 - V_3 - 11 = 0$

$11 = 14 - V_3$

$-V_3 = 11 - 14$

$\boxed{V_3 = 3 \text{ V}}$

no A:

$-I_3 + I_R - I_2 = 0$

$I_R = I_2 + I_3$

$I_R = 5 + \frac{V_3}{3}$

$I_R = 5 + \frac{3}{3} \quad \boxed{I_R = 6 \text{ A}}$

Logo: $V_{AC} = R \cdot I_R$

$R = \frac{V_{AC}}{I_R} = \frac{11}{6}$

$\boxed{R = 1,83 \Omega}$